



## 90-watt Audio Power Amplifier Stage

This is a simple, 90-watt, Quasi-complementary audio power amplifier. The final output transistors are paralleled 2N3055s, which deliver about about 90 wrms of clean power to an four-ohm load. The stages starts going into clipping when the input from the pre-driver reaches about 28 volts peak-to-peak.

Input, output and supply meters monitor current