



## Charge Pump Voltage Quadrupler

The 555 is configured in the astable mode, driving a four-node diode/capacitor ladder. Each cycle from the 555 builds the charge down the line, where it aggregates in C8. The 1k resistor at the output simulates the load.

Useful for bias supplies or programming voltages.

From "The Encyclopedia of Electronic Circuits".