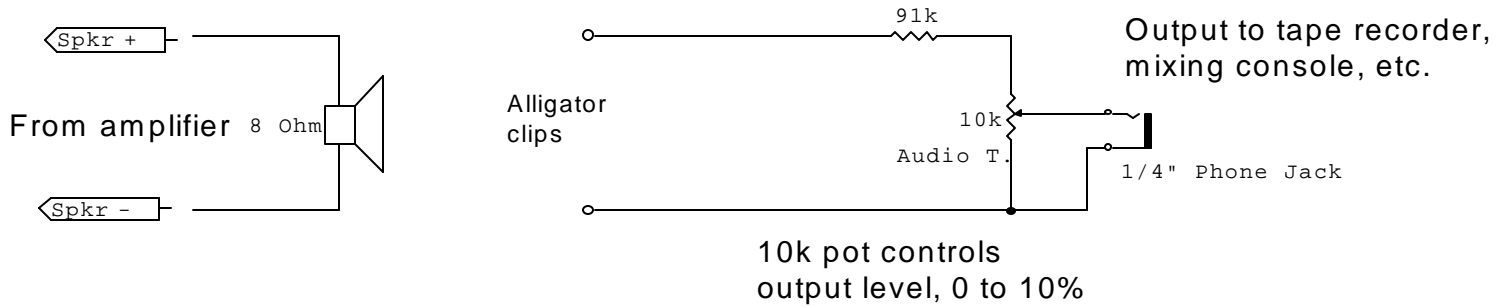


Alligator clips connect  
across loudspeaker  
leads



Minimum loss: 20db

### "10 to one Voltage Divider" for Direct Input

This simple voltage divider will allow you to record that sweet sound you can only get on your {fill in you favorite amp, here}, without having to use a microphone: Get your rig sounding the way you like it and then connect this across your speaker terminals; your amp won't even know it's there. Feed the output into a mixing board, or bus it into the monitor channel(s) so the horn section can hear your solos, too.

Keep one of these in your guitar bag until a recording engineer asks you for one.