



100 - 108 Mhz Wireless Microphone

This low-power FM transmitter will take sound input from the Electret Condenser Microphone and transmit it to a nearby FM radio tuned to a unused area of the dial in the 100 - 108 Mhz region. The microphone is very sensitive and will pick up a wisper in a room. The circuit is tuned with the 25 pf capacitor. Range can be up to 1/4 mile under ideal conditions